

## ECE 424 – INTRODUCTION TO VLSI DESIGN + LAB

### LABORATORY WORK 7

In this laboratory work, we will study on D flip-flops, T flip-flops and counters.

#### D-Flip Flop:

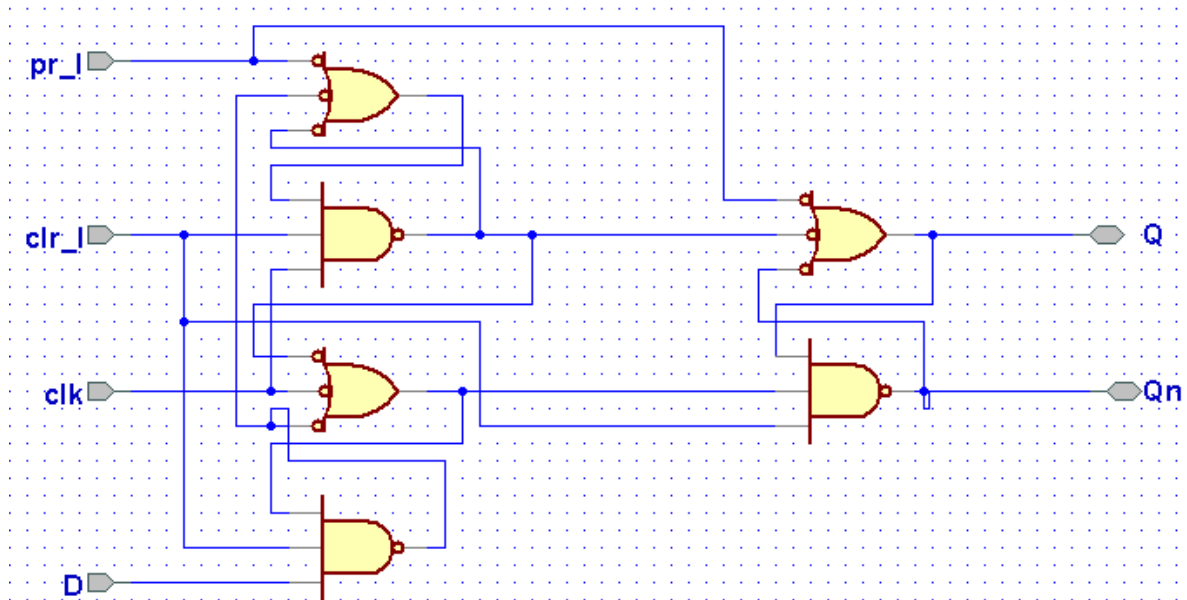


Figure 1 (D Flip Flop)

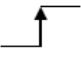
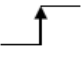
clr_1	pr_1	Clk	d	q	qn
0	0	X	X	1	1
0	1	X	X	0	1
1	0	X	X	1	0
1	1		0	0	1
1	1		1	1	0

Figure 2 (Truth Table)

```

library IEEE;
use ieee.std_logic_1164.all;
entity dff is
    port (
        pr_1: in STD_LOGIC;    -- active low preset input
        clr_1: in STD_LOGIC;    -- active low clear input
        clk :in STD_LOGIC;      -- clock input
        d   :in STD_LOGIC;      -- D input
        q   :inout STD_LOGIC;   -- output of D flip flop
        qn  :inout STD_LOGIC    -- inverted output
    );
end dff;
architecture dff of dff is
    signal e,f,g,h:std_logic;
    component nand3
    port (
        a,b,c: in STD_LOGIC;
        d   : out STD_LOGIC
    );
end component;
begin
    g1:nand3 port map(pr_1,h,f,e);    -- creates g1 gate
    g2:nand3 port map(clr_1,e,clk,f); -- creates g2 gate
    g3:nand3 port map(f,clk,h,g);     -- creates g3 gate
    g4:nand3 port map(g,clr_1,d,h);   -- creates g4 gate
    g5:nand3 port map(pr_1,f,qn,q);   -- creates g5 gate
    g6:nand3 port map(q,g,clr_1,qn);  -- creates g6 gate
end dff;

```

Figure 3 (VHDL Code for Dff)

```

library IEEE;
use IEEE.std_logic_1164.all;
entity nand3 is
    port (
        a,b,c: in STD_LOGIC;
        d   : out STD_LOGIC
    );
end nand3;
architecture \nand\ of nand3 is
begin
    d<= not (a and b and c); -- creates a 3 i/p nand gate
end \nand\;

```

Figure 4 (3-input nand gate)

Write thee codes and simulate it by using computer. Try to understand the working principles of the code. Then, write D flip flop behavioral codes.

## T Flip-Flop:

 


Figure 5 (T Flip Flop)

```
library IEEE;
use IEEE.std_logic_1164.all;

entity tff is
    port (
        t      : in STD_LOGIC;--input to the T-flip flop
        clk    : in STD_LOGIC;--Clock signal for T-flip flop
        clr_1  : in STD_LOGIC;--active low clear input
        q,nq   : out STD_LOGIC--actual and complemented outputs of T-flip flop
    );
end tff;

architecture tff of tff is
begin
    process(t,clk,clr_1)
        variable temp:STD_LOGIC:='0';
    begin
        if (clr_1='0') then
            temp:='0';

        elsif ((clr_1='1') and (clk'event and clk='0')) then--performs during falling edge
            if ( t='0') then
                temp:=temp;
            else temp:= not temp;
            end if;
        end if;
        q<= temp;
        nq<= not temp;
    end process;
end tff;
```

Figure 6 ( Behavioral Code of T flip-flop)

Write this code in a new project and simulate it. Don't delete it, you will use it in next part.

## 4 – Bit Binary Counter:

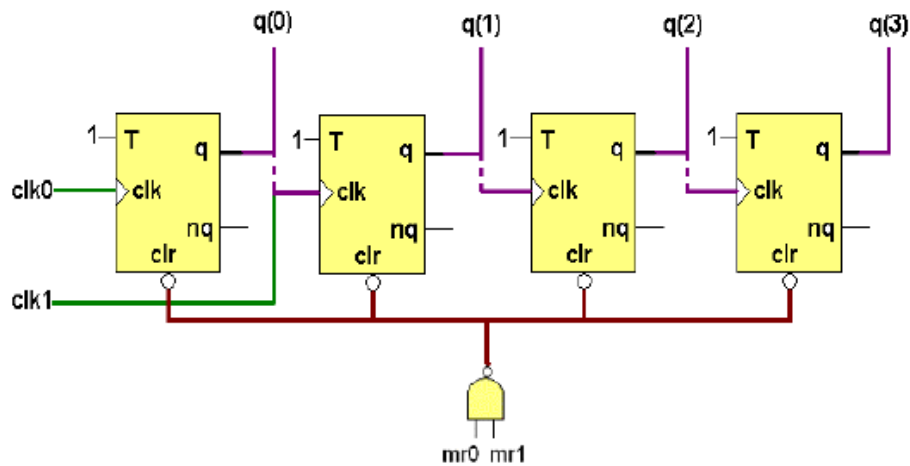


Figure 7 (4 - Bit Binary Counter)

```

library IEEE;
use IEEE.std_logic_1164.all;

entity cnt is
    port (
        clk0: in STD_LOGIC;
        mr0: in STD_LOGIC;
        mr1: in STD_LOGIC;
        clk1: inout STD_LOGIC;
        Q: inout STD_LOGIC_VECTOR(3 downto 0)
    );
end cnt;

architecture cnt of cnt is

    Component tff -- T- flip flop instantiation
    port (
        t : in STD_LOGIC;
        clk : in STD_LOGIC;
        clr_1 : in STD_LOGIC;
        q,nq : out STD_LOGIC
    );
end component;
signal clear : std_logic;
begin
    clear<= mr0 nand mr1; -- common reset inputs for mod2 and mod8
                        --counters
    CLK1<=q(0); --to work as asynchronous mod16 counter
    t1:tff port map('1',clk0,clear,Q(0),open);--t1,t2,t3,t4 create four T-flip flops
    t2:tff port map('1',clk1,clear,Q(1), open);
    t3:tff port map('1',Q(1),clear,Q(2), open);
    t4:tff port map('1',Q(2),clear,Q(3), open);

end cnt;

```

Figure 8 (VHDL Codes for 4-bit counter)

Write the code and simulate it.

**Homework:** Write N-bit counter by using “generic” method. Make a research about the usage of this method and write a behavioral code for N bit counter.

(For simulation, you can take  $N=8$ ).

**Send me whole project folders. (Not screenshots or just codes)**

**Deadline: 24.12.2013 Tuesday, 21:00.**

**No late submission is going to be accepted!**

*Prepared By: İbrahim BOZKURT*  
*e-mail: [ibrahimbozkurt@cankaya.edu.tr](mailto:ibrahimbozkurt@cankaya.edu.tr)*