

ECE 424 Introduction to VLSI


Home Work 1 (Due to 03.11.2014)

NOTE: In the following problems, assume $T = 300\text{ K}$.


Q1) Plot the I_d versus V_{ds} (for different V_{gs} voltages) characteristics, for an n-channel MOS transistor of $L=150\text{nm}$, $W=800\text{ nm}$, mobility= $1830\text{ cm}^2/\text{Vs}$, relative permittivity= 11.7 , $t_{ox}=120\text{ angstrom}$, using MATLAB. **NOTE:** Print out your results and explanations (including MATLAB codes) for this problem.

 Q2) The depletion load NMOS inverter below is biased at $V_{DD}=3\text{V}$. The transistor parameters are $k'_n=60\mu\text{A}/\text{V}^2$, $(W/L)_D=6$, $(W/L)_L=2$, $V_{TND}=0.4\text{V}$, and $V_{TNL}=-0.8\text{V}$.

- Determine v_o for $v_i=3\text{V}$.
- Find the transition points for the driver and the load.
- Calculate the power dissipation in the inverter for $v_i=3\text{V}$.



 - Q3) (a) Redesign the resistive load inverter below so that the maximum power dissipation is 0.25 mW with $V_{DD} = 3.3\text{ V}$ and $v_o = 0.15\text{ V}$ when the input is a logic 1.
- (b) Using the results of part (a), what is the input voltage range when the transistor is biased in the saturation region? Assume transistor parameters of $V_{TN} = 0.5\text{ V}$ and $k'_n = 100\mu\text{A}/\text{V}^2$.



Q4) The NMOS inverter with depletion load above is biased at $V_{DD} = 2.5$ V. The transistor parameters are $V_{TND} = 0.5$ V and $V_{TNL} = -1$ V. The width-to-length ratio of the load device is $W/L = 1$. Assume $k'_n = 100 \mu\text{A}/\text{V}^2$.

- (a) Design the driver transistor such that $v_O = 0.05$ V when the input is a logic 1.
- (b) What is the power dissipated in the circuit when $v_I = 2.5$ V?