
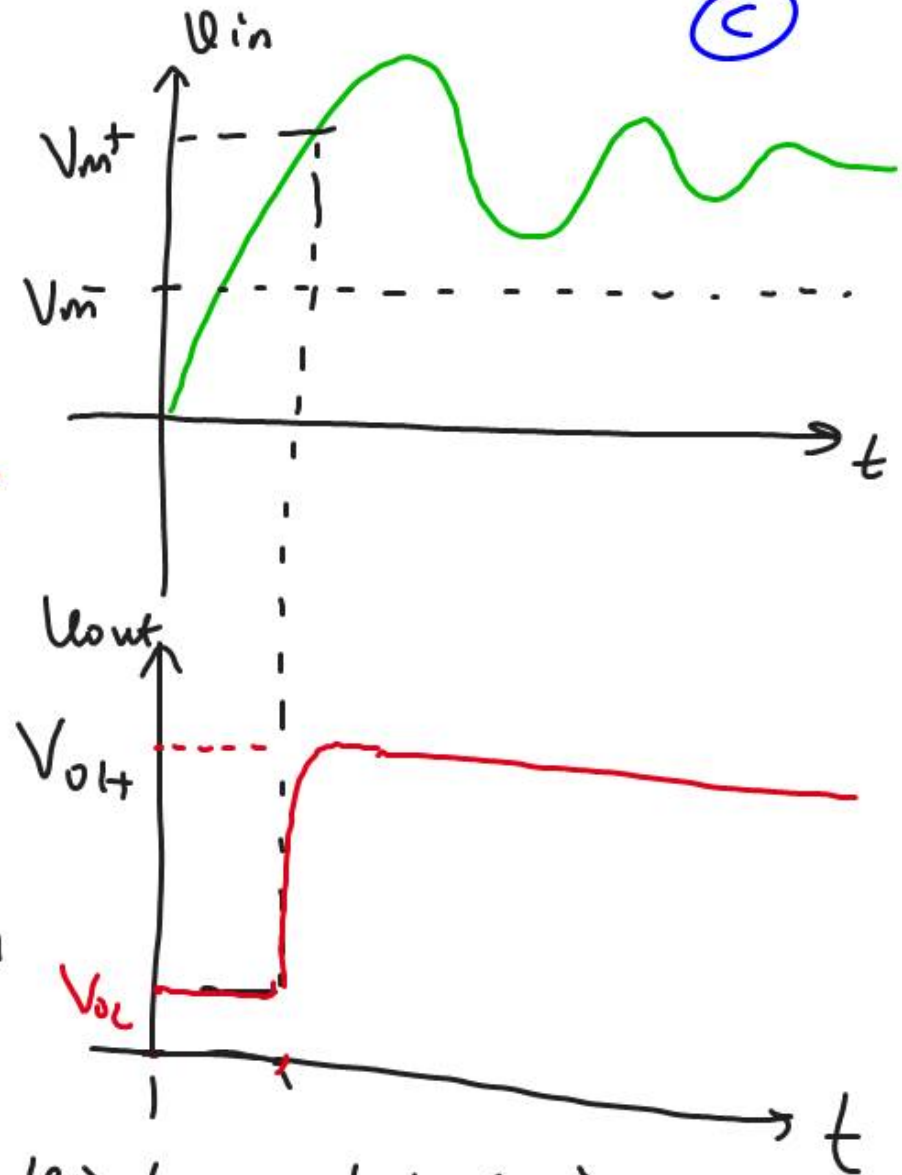


SCHMITT TRIGGER


24.12.2010

©

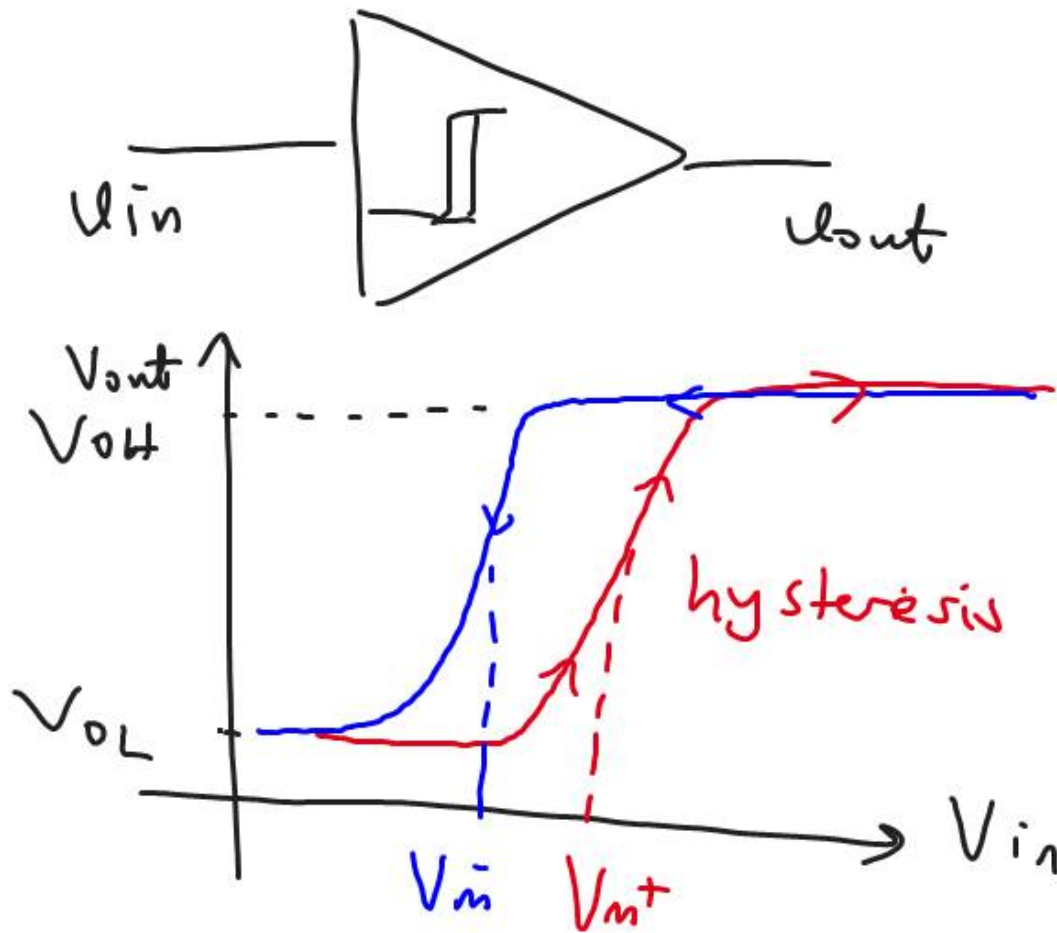


Although V_{in} has a lot of noise, the output signal will be very clean.

MONOSTABLE CIRCUIT

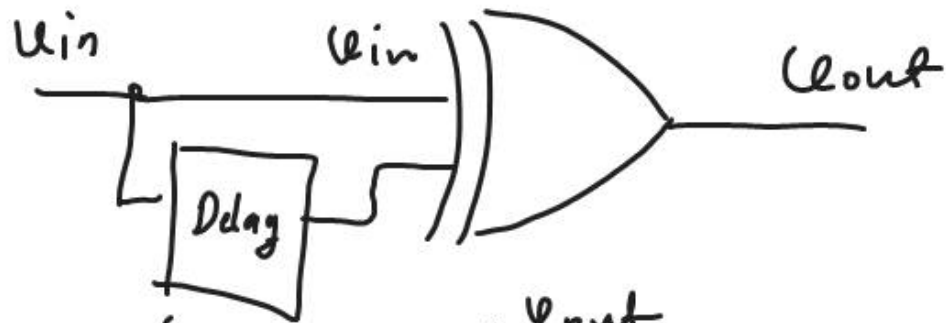


a	b	f
0	0	0
0	1	1
1	0	1
1	1	0

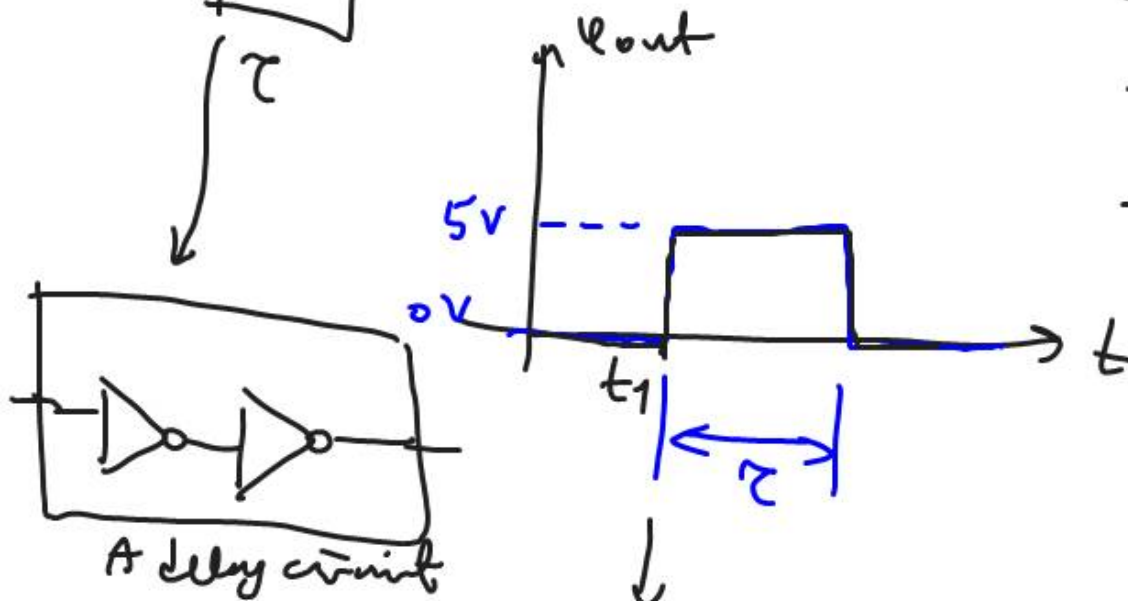


at $t = t_1$ we apply U_{in}

A VOLTAGE-CONTROLLED OSCILLATOR

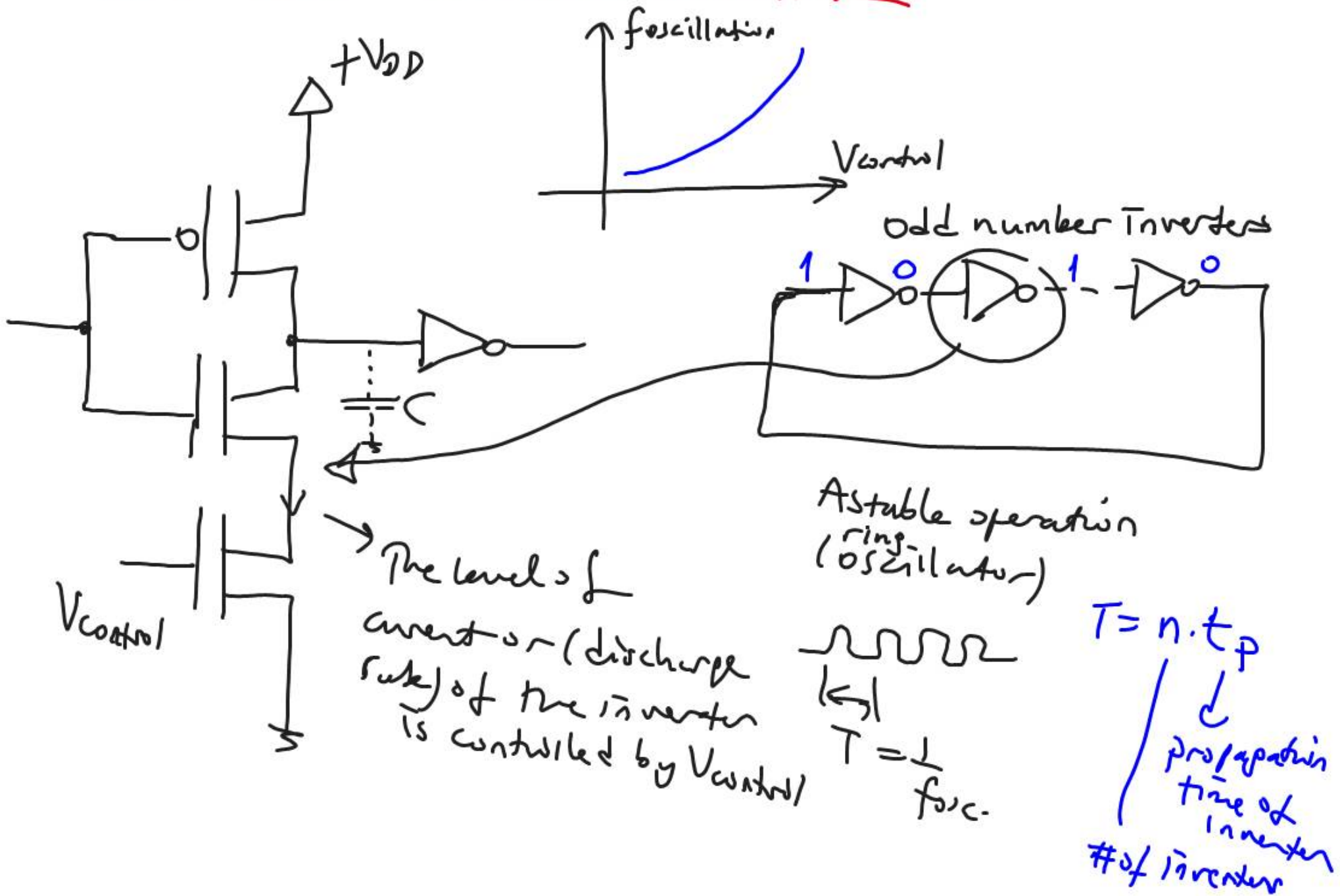


REGISTERS

SHIFT REGISTER

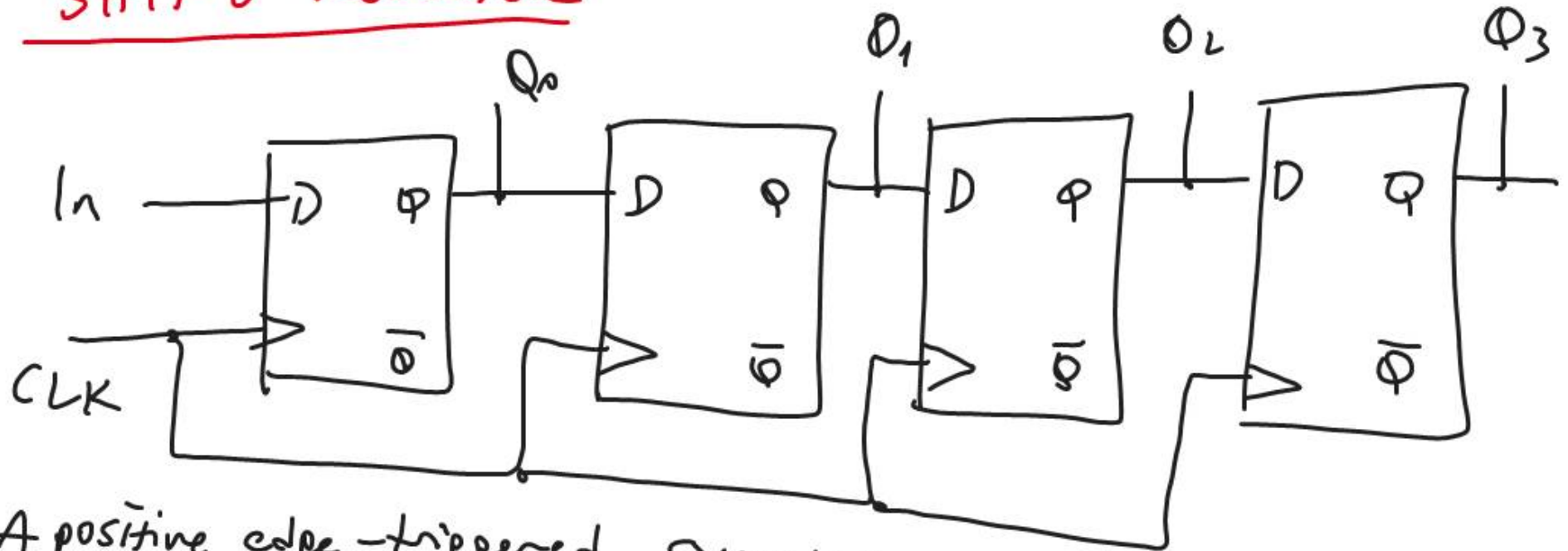


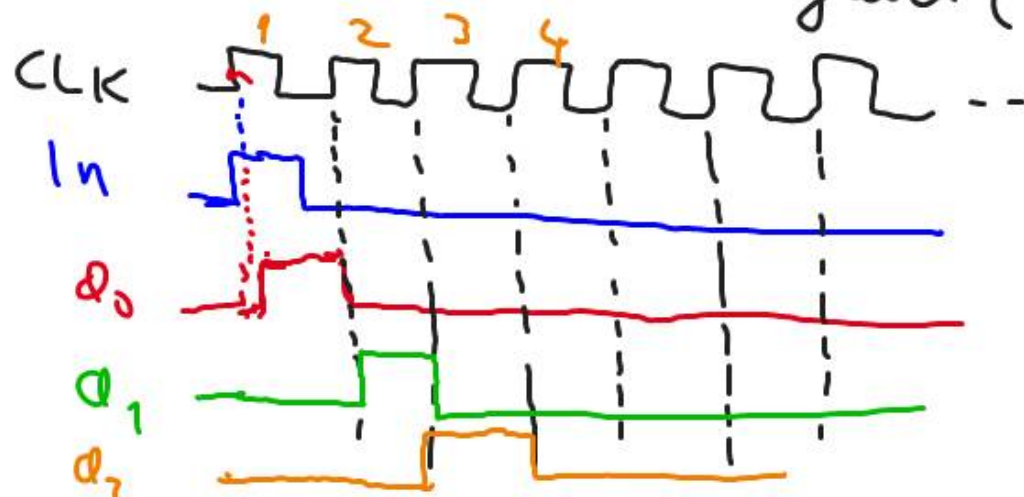A positive edge-triggered SYNCHRONOUS Register (4-bit)




Shift Register with Data Load register

Select	
0	Shift Right
1	Data Load

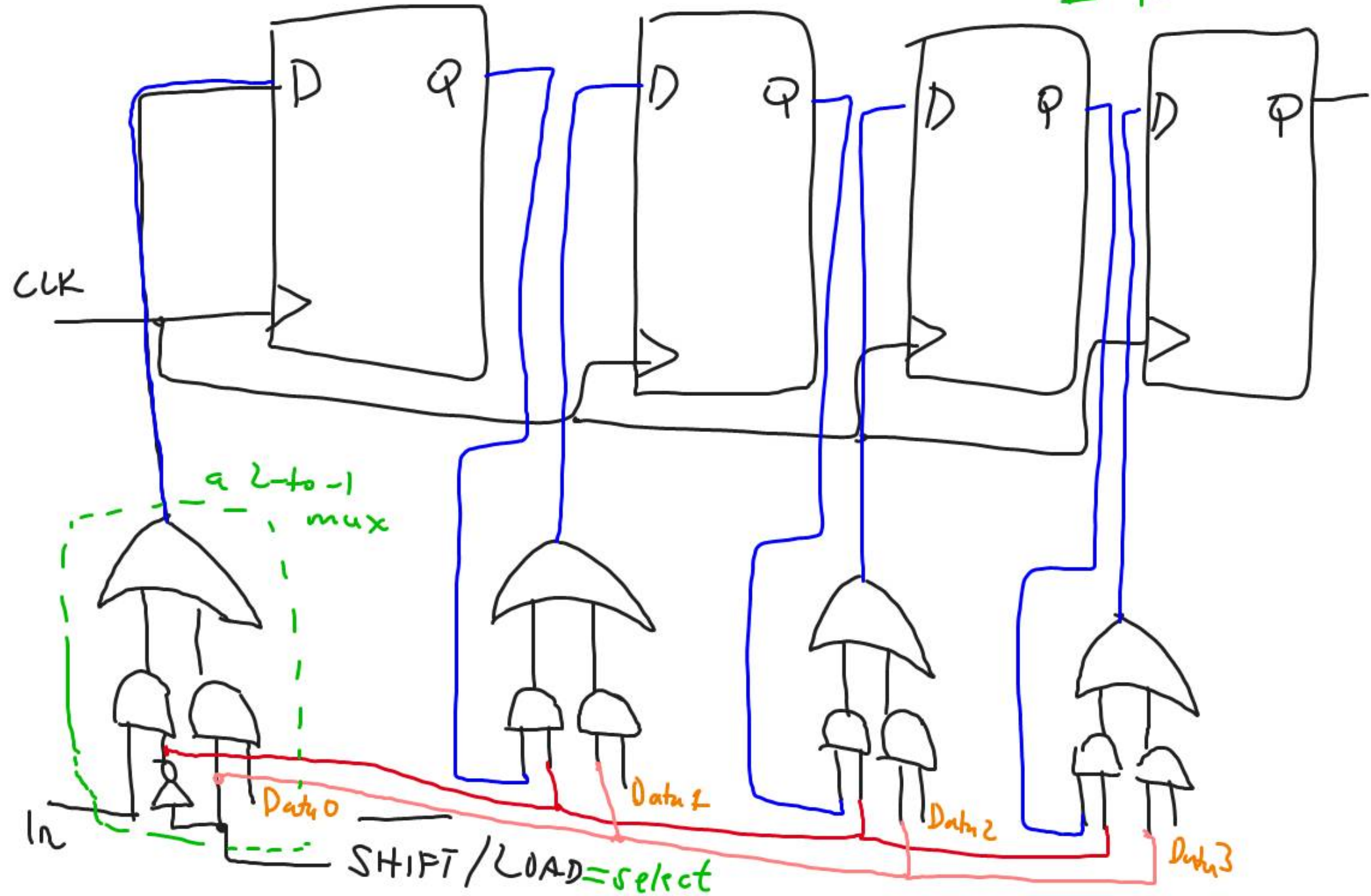


S1	S0	
0	0	Shift RIGHT
0	1	DATA LOAD
1	0	RESET
1	1	Shift LEFT

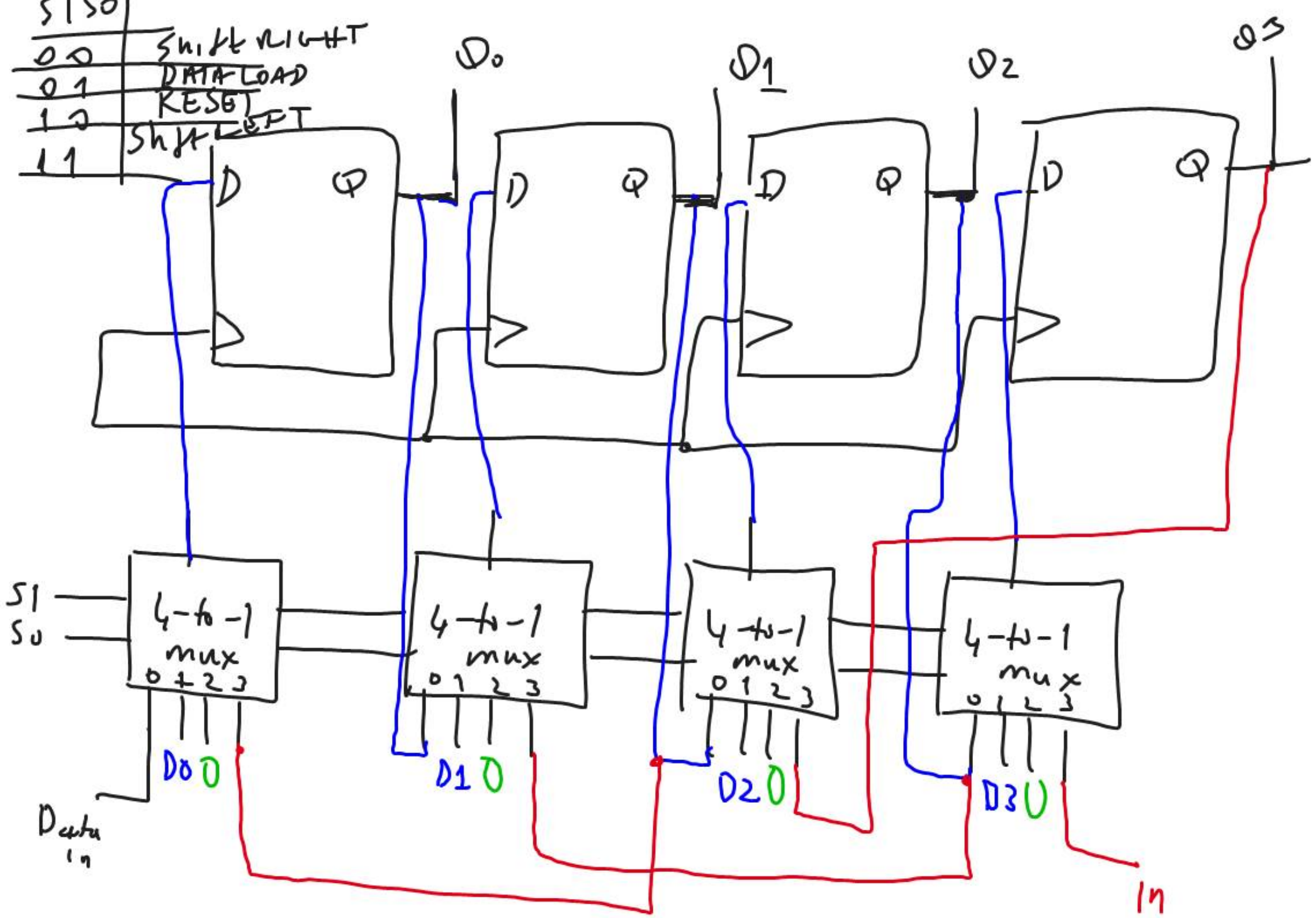

COUNTERS


ASYNCHRONOUS COUNTERS (Ripple counters)

T flip flops are used, (generally)

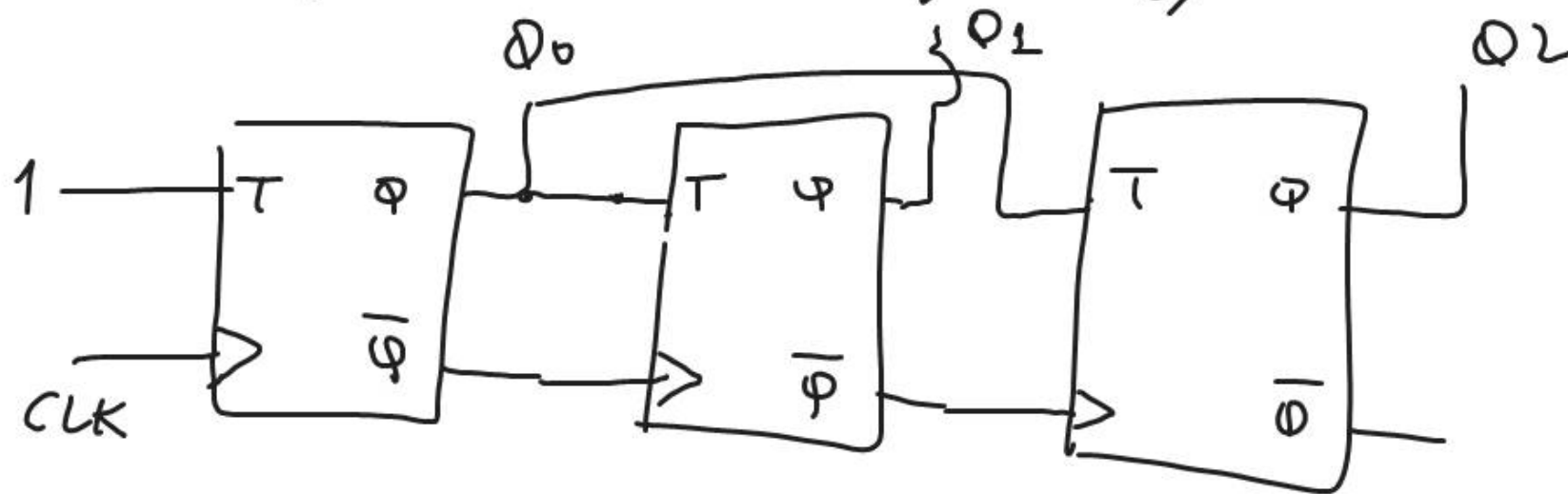


up-counter with T flip flops

T	Q_n	
0	Q_{n-1}	Holds
1	$\overline{Q_{n-1}}$	Toggles

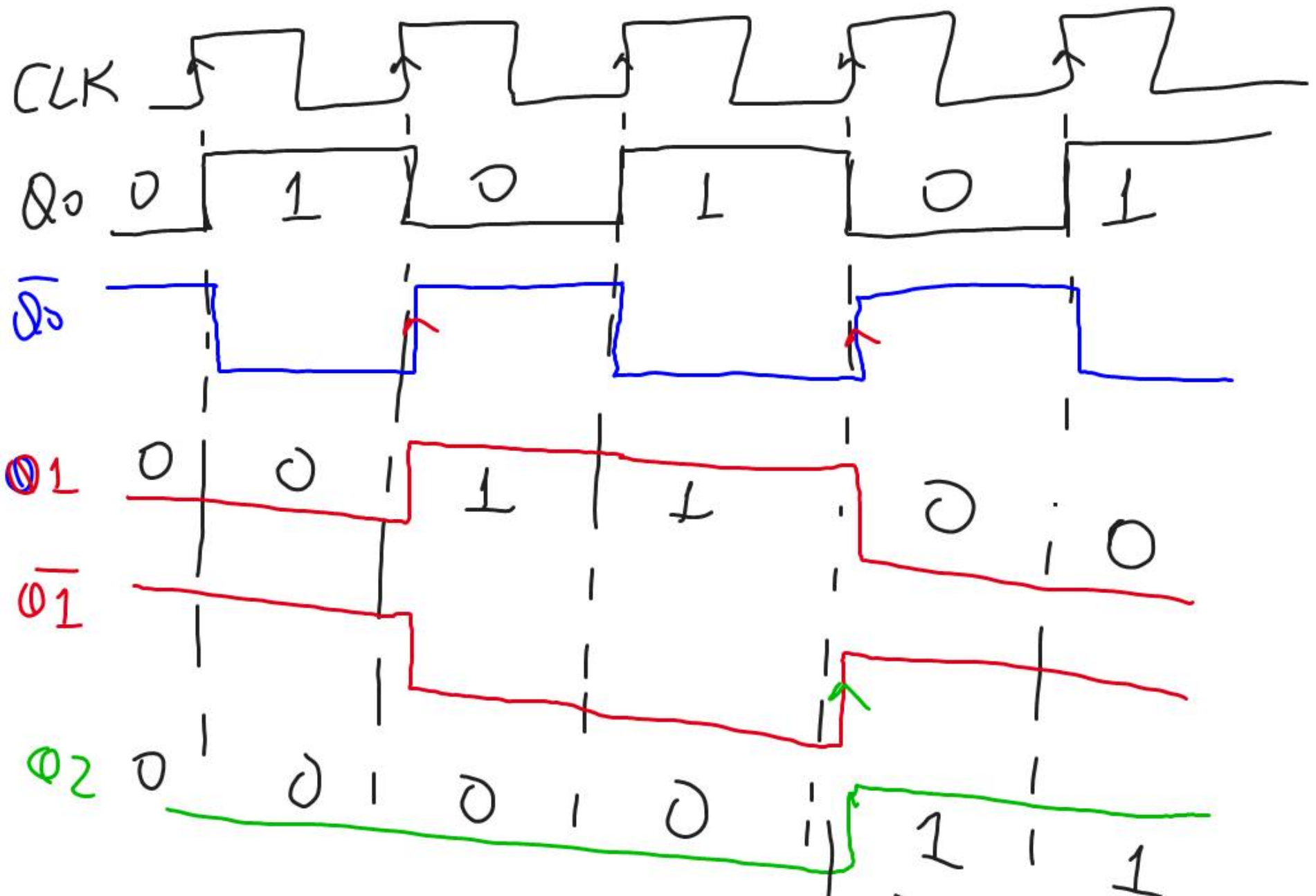

↓ Ripple. Accumulation of propagation times of CLK signal

Count-down Ripple Register Counter

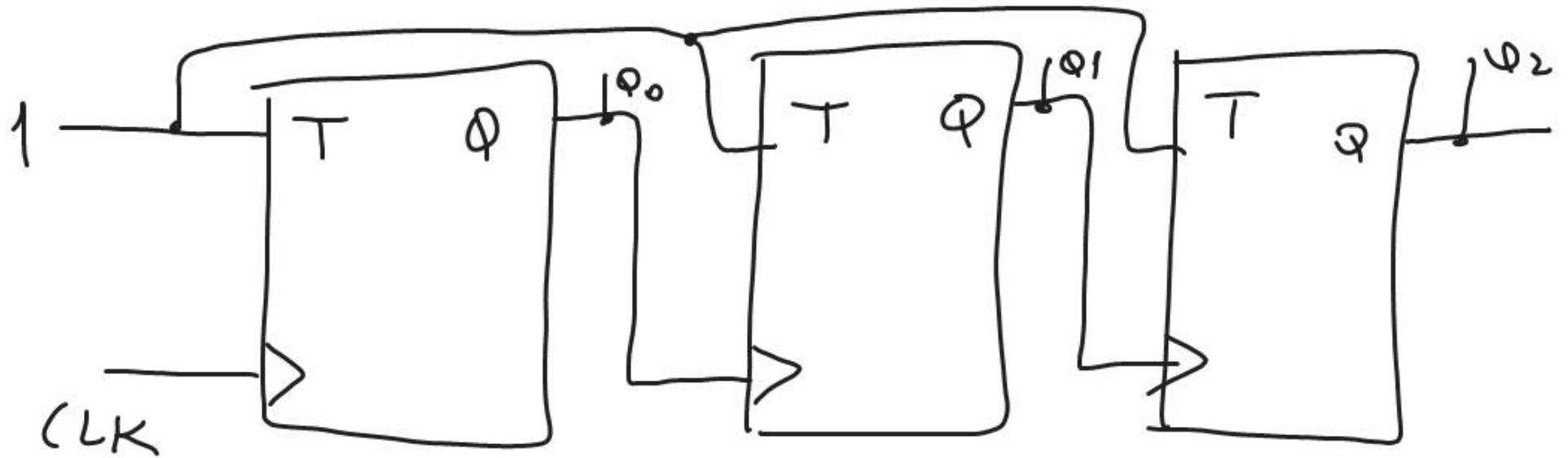

SYNCHRONOUS COUNTERS

Clock signal is applied at the same time to all ^{flip-flops} registers.

They do not have Clock RIFFLE problems.

They can be designed in a regular method.

Present State, Next States

Q_2	Q_1	Q_0	T_2	T_1	T_0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	0	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	1	0	1	1
1	1	0	0	0	1
1	1	1	1	1	1


$T_0 = 1$

T_1	Q_2	00	01	11	10
0	0	0	1	1	0
1	0	0	1	1	0


$T_2 = Q_1 \cdot Q_0$

$T_1 = Q_0$


Q_2	$Q_1 Q_0$	00	01	11	10
0	0	0	0	1	0
1	0	0	0	1	0

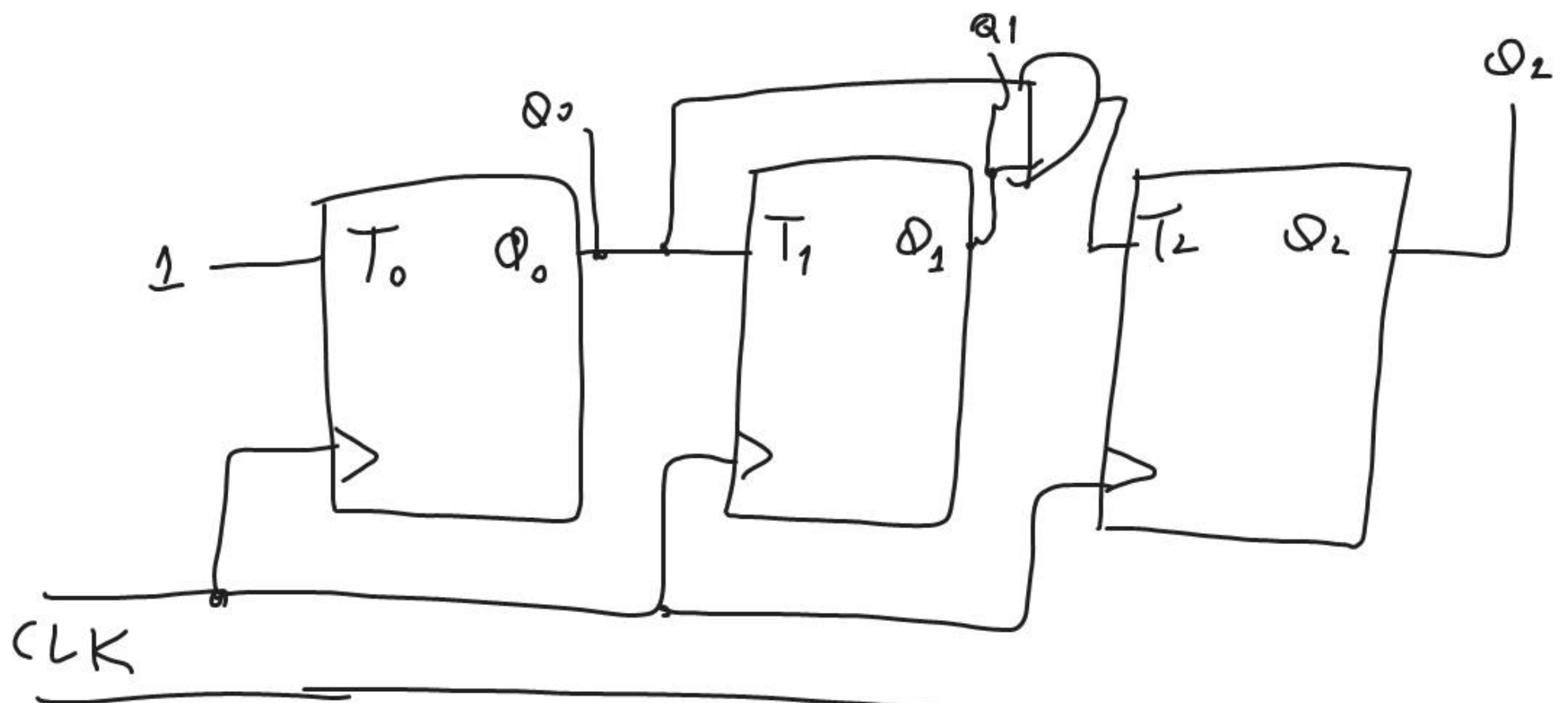


It is a Finite State Machine (FSM)

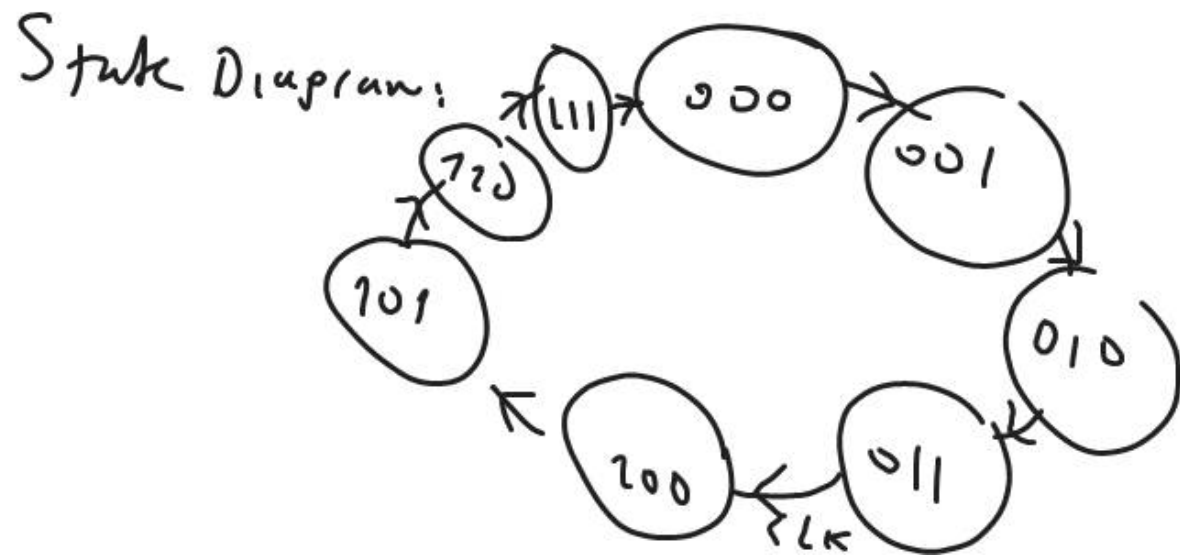


Example:

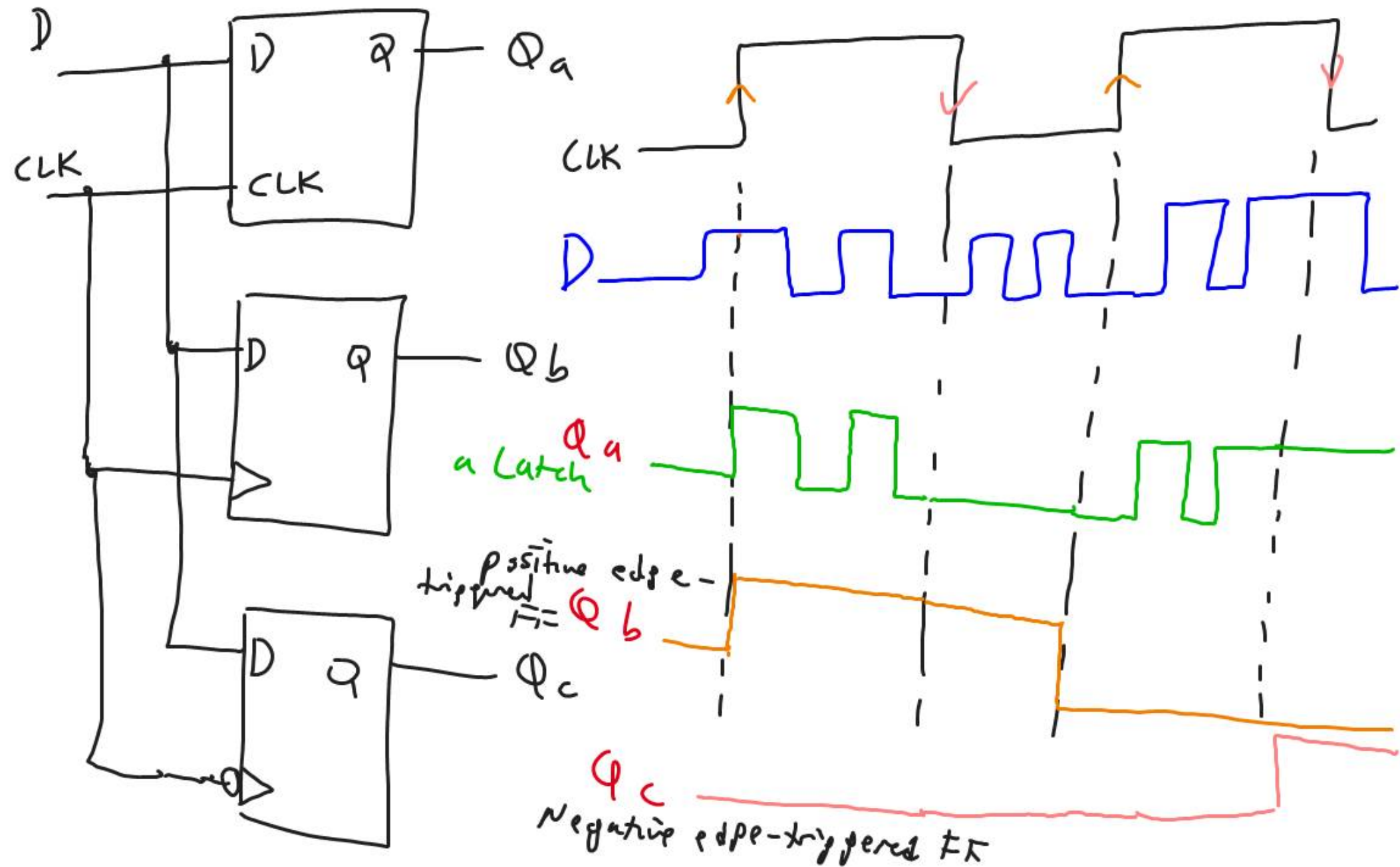

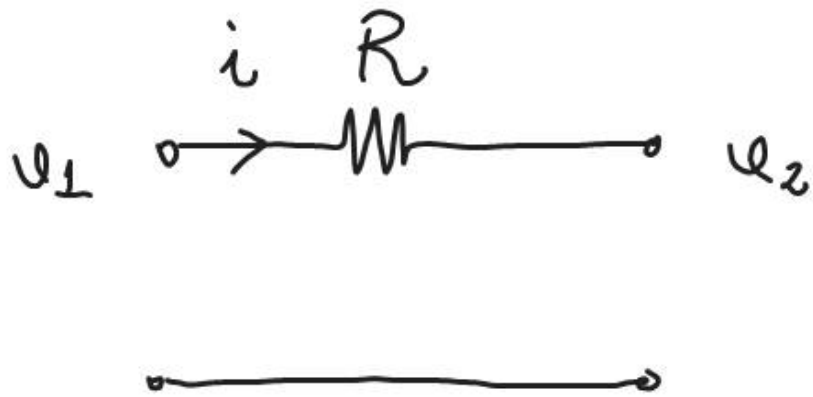A Switched Capacitor acting as a Resistor




?

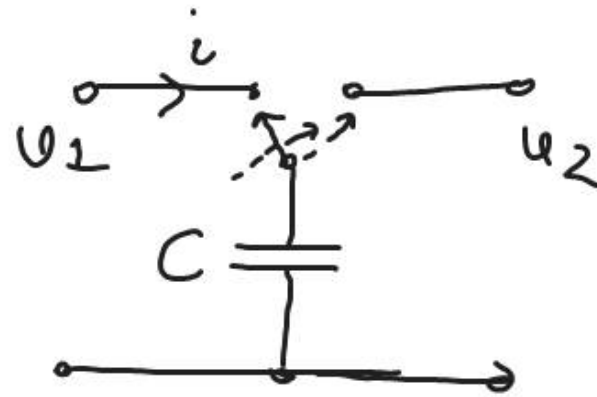


The charge transferred by the capacitor in 1 period of switching

$$Q = CV$$

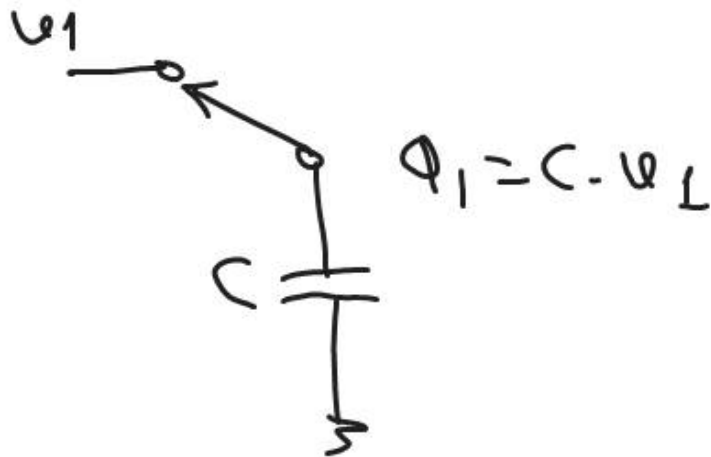

$$Q = C(v_1 - v_2)$$

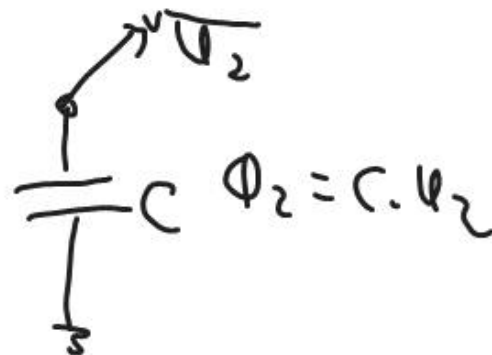

$$Q_1 - Q_2 = C(v_1 - v_2)$$

$$i = \frac{dq}{dt} \approx \frac{\Delta q}{\Delta t} = \frac{C(\phi_1 - \phi_2)}{T}$$

switching period

$$i = \frac{\phi_1 - \phi_2}{R}$$

when we have
the resistor

$$i = \frac{C(\phi_1 - \phi_2)}{T}$$

when we have the
switched capacitor

$$\frac{\cancel{\phi_1 - \phi_2}}{R} = \frac{C(\cancel{\phi_1 - \phi_2})}{T}$$

$$\boxed{R = \frac{T}{C}}$$

if we select the C and T properly
we obtain the required resistance

In integrated circuit $\Rightarrow$ manufacturing transistors and capacitors are preferred to manufacturing R and L.

