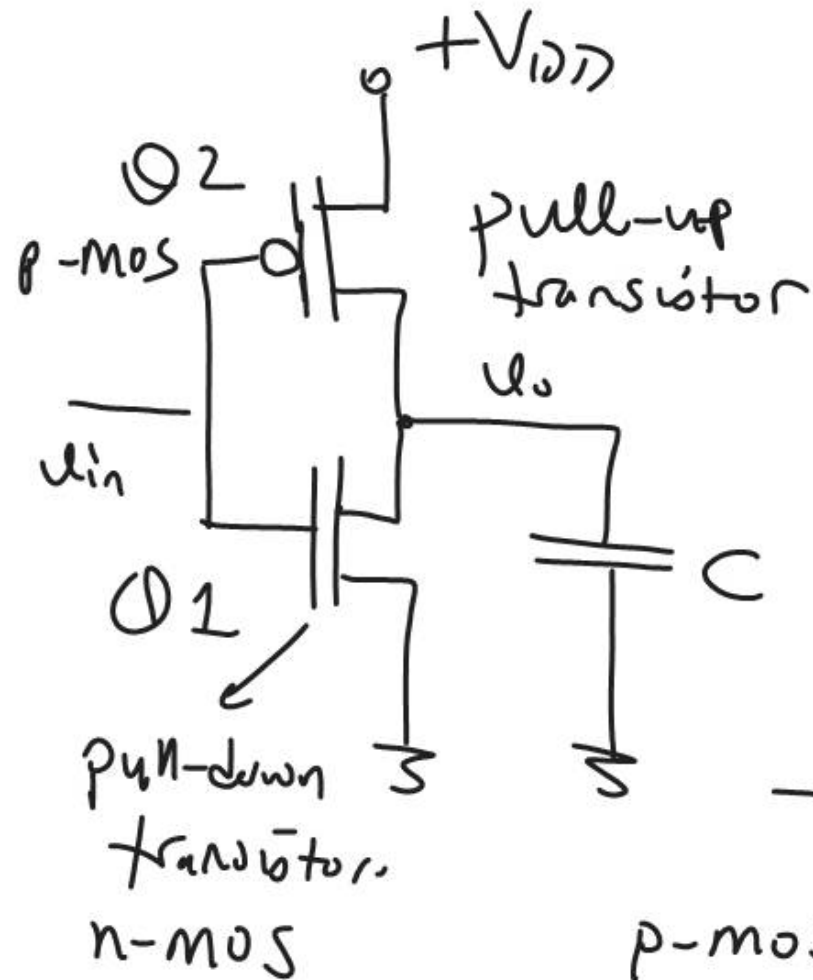


15.10.2010 ©




Power (energy) consumption :



When $V_{in} = V_{DD}$ (1)

$$u_o \approx 0$$

Q1 is ON
Q2 is OFF

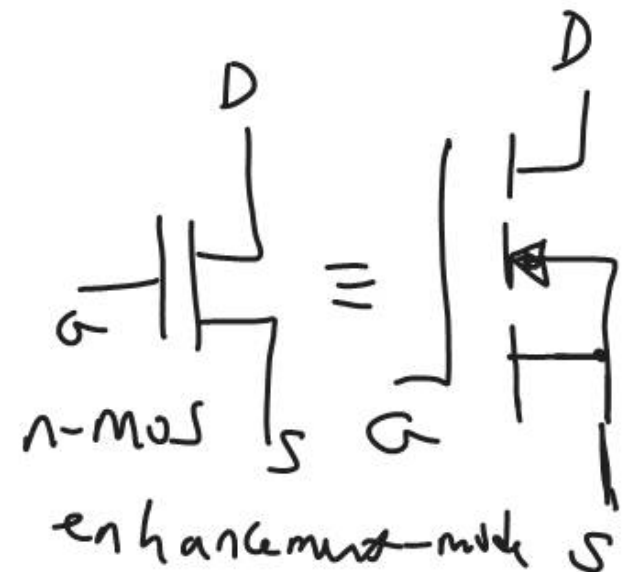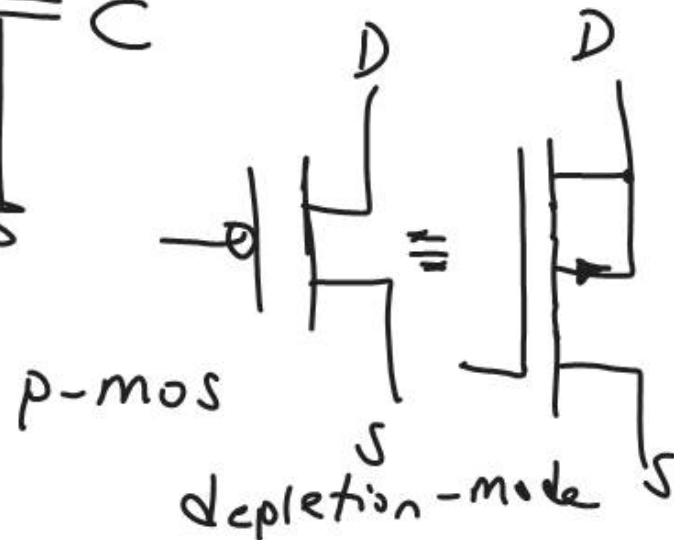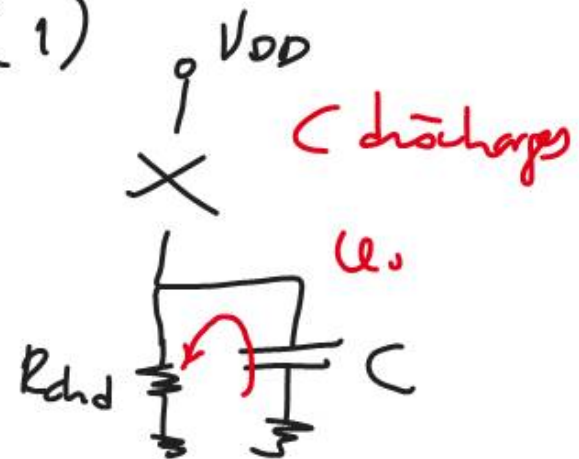


$$V_{in} = 0$$

$$V_o = V_{DD}$$

$$Q2 = ON$$

$$Q1 = OFF$$

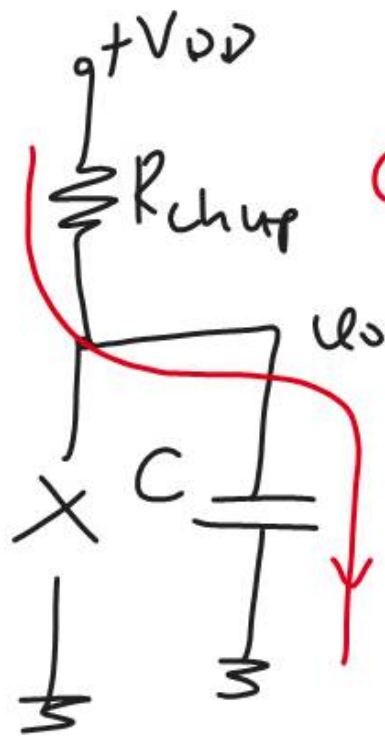

C is charged.

The energy (total) consumed from the Power supply:

$$E_{io} = \int_0^{\infty} i(t) \cdot V(t) \cdot dt$$

Instantaneous current drawn from power supply

Instantaneous voltage of power supply

$$V(t) = V_{DD}$$

Power supply voltage is assumed to be constant

$$E_{in} = V_{DD} \int_0^{\infty} \bar{i}(t) dt$$

$$\bar{i}(t) = C \cdot \frac{dV_{out}}{dt}$$

$$E_{in} = V_{DD} C \int_0^{\infty} \frac{dV_{out}}{dt} dt$$

$$= V_{DD} C \int_0^{V_{DD}} dV_{out}$$

$$E_{in} = C \cdot V_{DD}^2$$

x Energy used is not dependent on the R .


To reduce Energy Consumed

(1) V_{DD} (PS voltage) should be reduced, if possible

(2) The capacitance (C) should be minimized, if possible

How This energy is dissipated?

① CHARGING

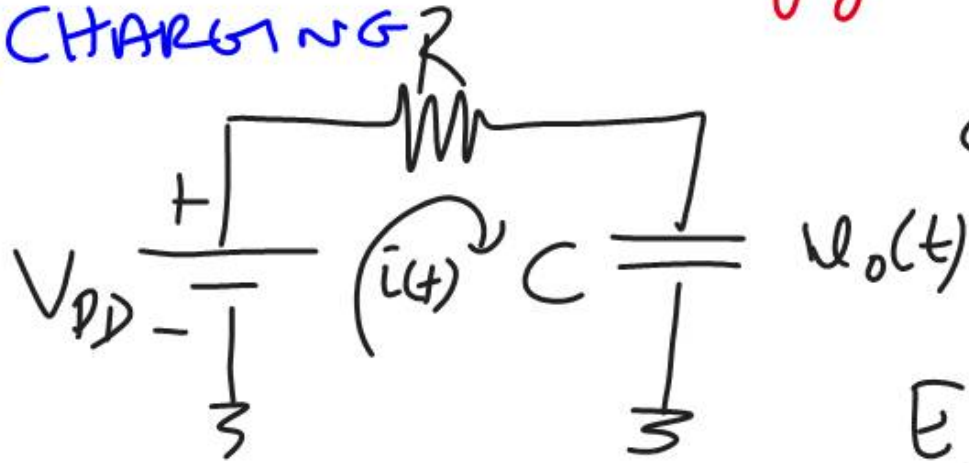

Charging

$$E_{\text{dissipated}} = \int_0^{\infty} i(t) \cdot V_O(t) dt$$

This energy is
dissipated as ~~HEAT~~
on the R !


Power $\Rightarrow i^2 \cdot R$
dissipated $\frac{V_C}{R}$

$$\begin{aligned} E_{\text{dissipated}} &= C \int_0^{\infty} \frac{dV_{\text{out}}}{dt} \cdot V_{\text{out}} dt \\ &= C \int_0^{V_{DD}} V_{\text{out}} dV_{\text{out}} \end{aligned}$$

$$E_{\text{dissipated}} = \frac{C V_{DD}^2}{2}$$

(Lost)

② DISCHARGING

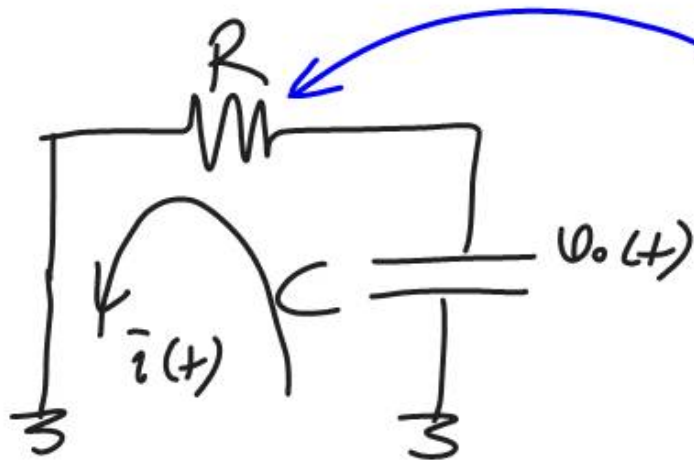

$$E_{\text{dissipated}} = \frac{C V_{0D}^2}{2}$$

as heat on the R !

2 ~~M~~ transistors $\rightarrow$ dissipate a lot of energy
in a chip
on a very limited area
(size of the die)

$$C = 10^{-14} \text{ F} \quad V_{DD} = 5V \quad E_{in} = C V^2 = 10^{-14} \cdot 25 = 25 \times 10^{-14} \text{ Joule}$$

$$\text{Total } E_{in} = 2 \times 10^6 \times 10^{-14} \cdot 25 = 5 \times 10^{-2} \text{ Joule}$$

If the clock cycle is 2 GHz

$$T = \frac{1}{2 \times 10^9} \approx 0.5 \times 10^{-9} \text{ s.}$$

$$P = \frac{5 \times 10^{-7} \text{ J}}{0.5 \times 10^{-9} \text{ sec.}}$$


$$\underline{P = 1000 \text{ W!}}$$

Area of the chip: $2.5 \text{ mm} \times 1.5 \text{ mm} = 2.25 \text{ mm}^2$

$$\frac{E}{\text{Area}} = \frac{5 \times 10^{-7} \text{ Joules}}{2.25 \times 10^{-6} \text{ m}^2} \approx 0.2 \text{ J/m}^2$$


HEAT SINKING

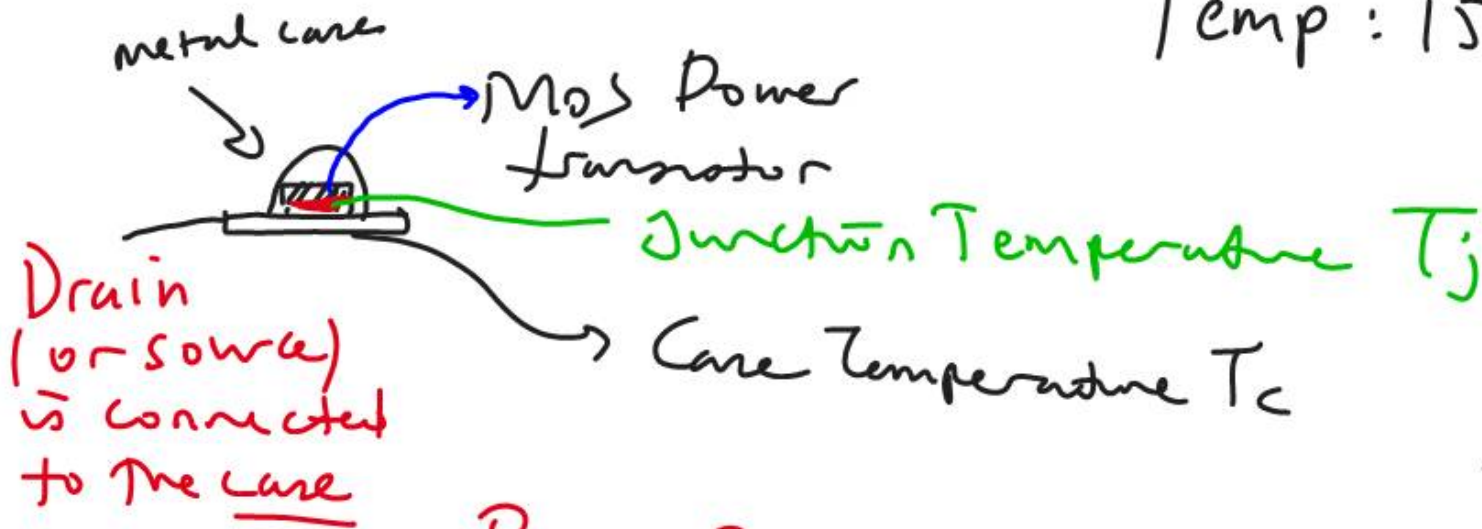Si Transistors Max Junction Temp : $150 - 200^{\circ}\text{C}$



Heat resistance between junction and case is
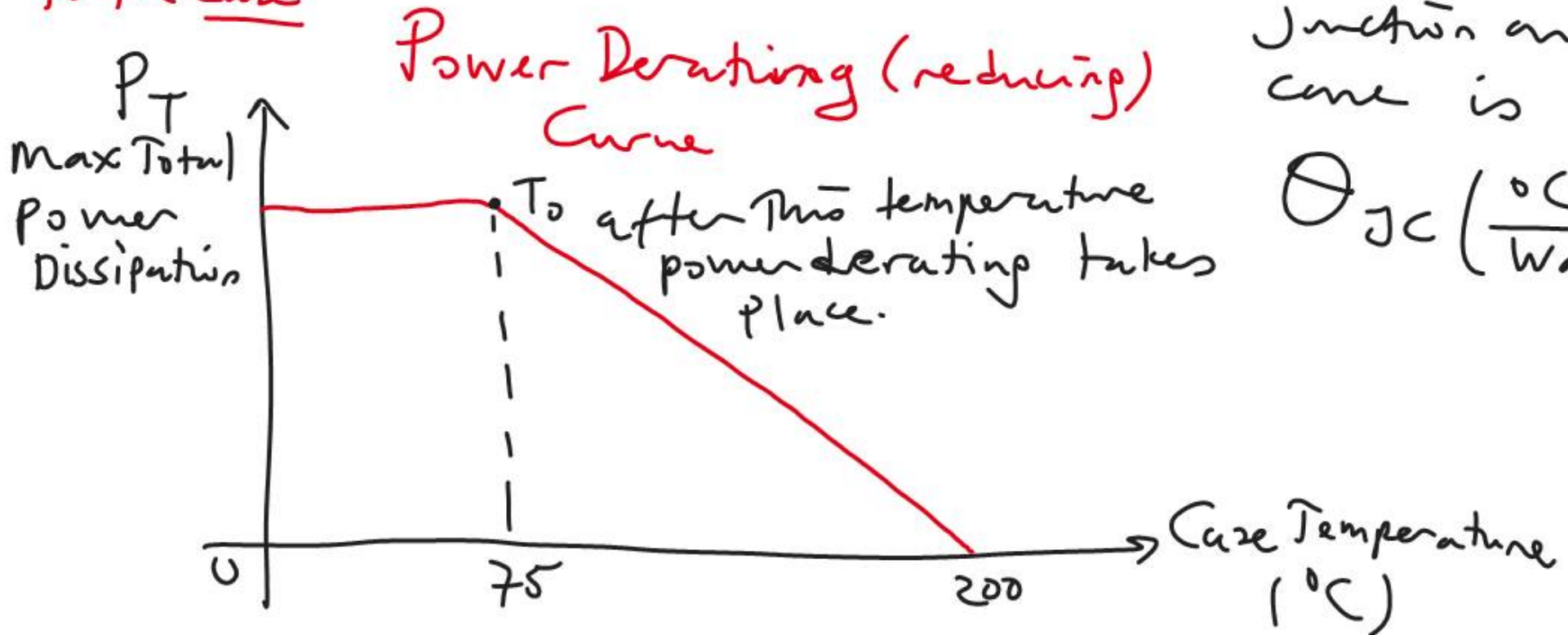
$$\theta_{JC} \left(\frac{^{\circ}\text{C}}{\text{Watt}} \right)$$



$$T_J - T_C = \Theta_{JC} \cdot P_D$$

another representation of power derating curve.


$$\Theta_{JC} \approx 0.5^\circ\text{C}/\text{W}$$

$$\text{if } P_D = 50\text{W}$$

$$T_J - T_C = 0.5 \frac{^\circ\text{C}}{\text{W}} \cdot 50\text{W}$$

$$T_J - T_C = 25^\circ\text{C}$$

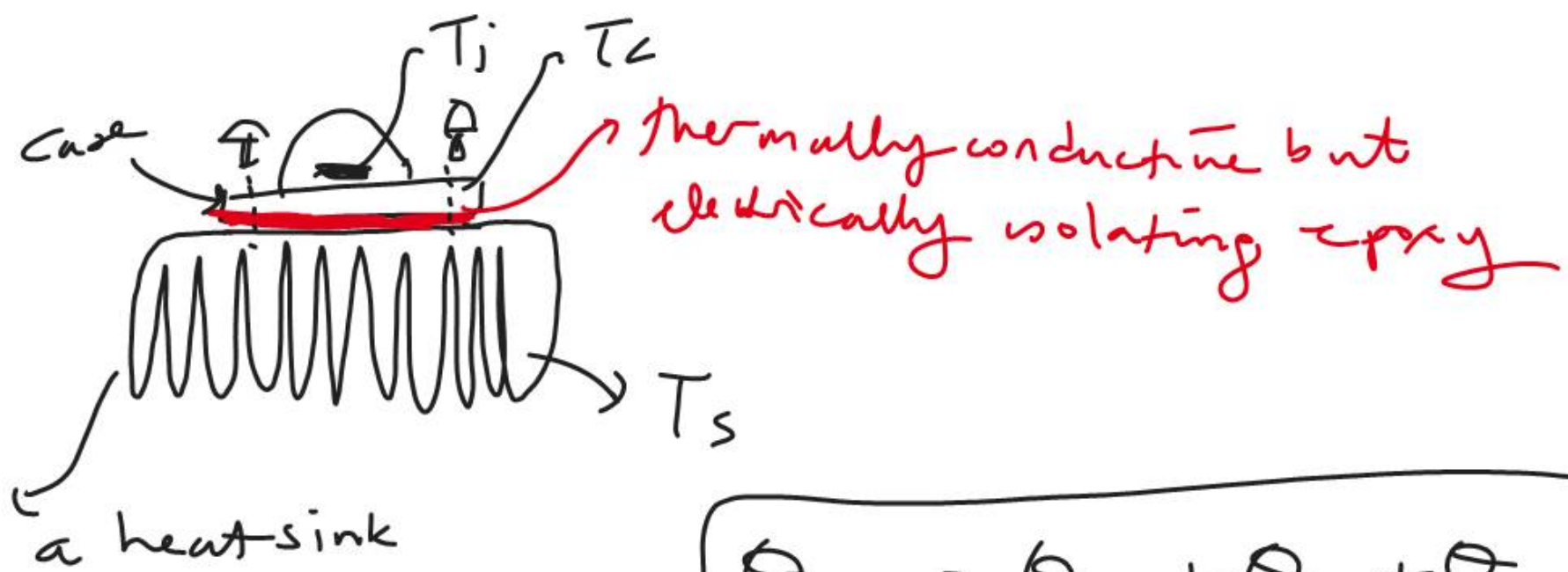means if the case is ^{at} $50^\circ\text{C} \rightarrow$ then junction is at 75°C



$$\Theta_{JA} = \Theta_{JC} + \Theta_{CS} + \Theta_{SA}$$

if there were no heat sink $\Theta_{JA} = 40^\circ\text{C/W}$

$P_D = 20\text{W}$

$$T_j - T_a = 20 / 40^\circ\text{C/W} = \underline{800^\circ\text{C}}$$

$$P_D = 1\text{W} \quad T_j - T_a = 1 \times 40 = \underline{40^\circ\text{C}}$$

If we use heat sink of $\theta_{SA} = 3^\circ\text{C/W}$

$$\theta_{JC} = 0.8^\circ\text{C/W}$$

$$\theta_{CS} = 0.5^\circ\text{C/W}$$

$$\theta_{SA} = 3^\circ\text{C/W}$$



$$\theta_{JA} = 0.8 + 0.5 + 3 = 4.3^\circ\text{C/W}$$

for $P_D = 20\text{ W}$



$$T_J - T_A = 20 \cdot 4.3^\circ\text{C/W} \approx 86^\circ\text{C}$$


$$\text{If } \underline{T_A = 20^\circ\text{C}} \quad \underline{T_J = 106^\circ\text{C}}$$

THE INVERTER

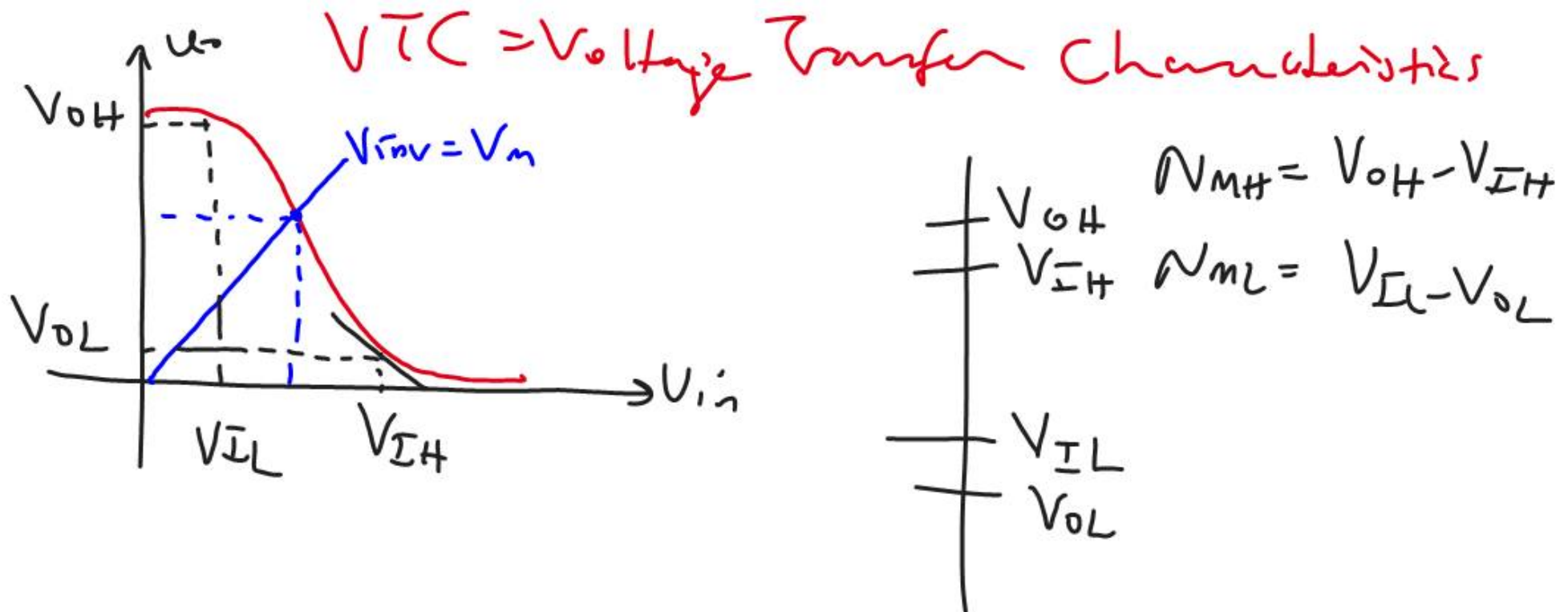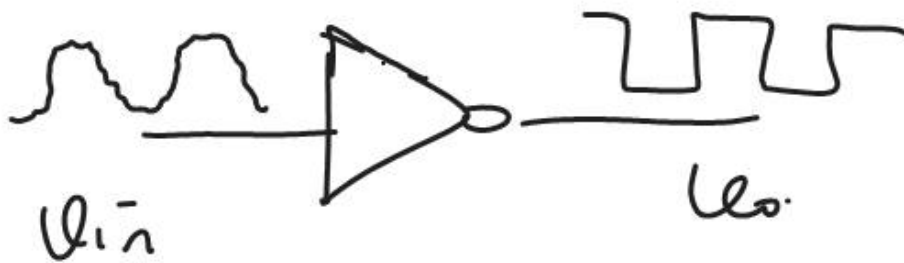



Types of Inverters

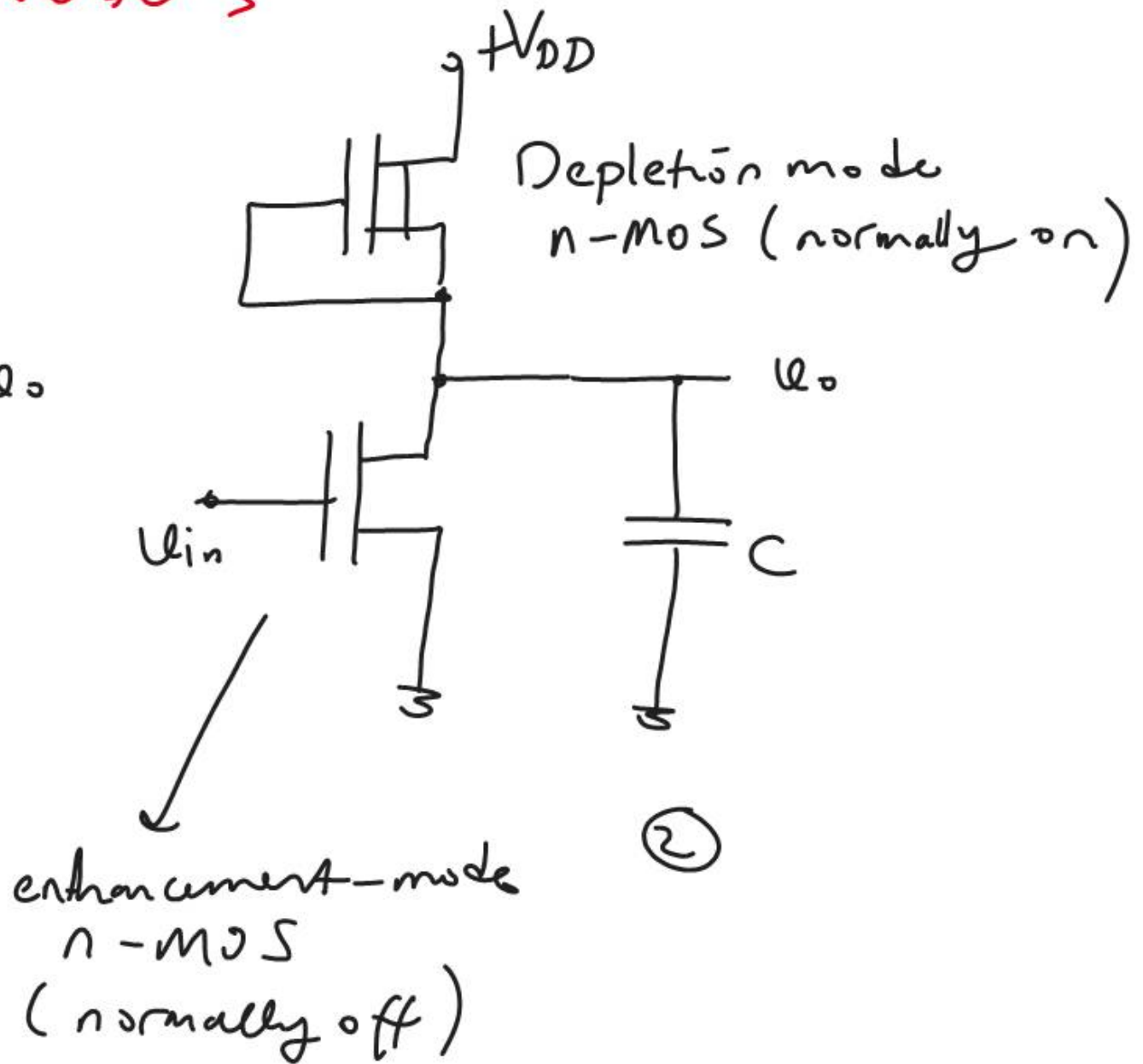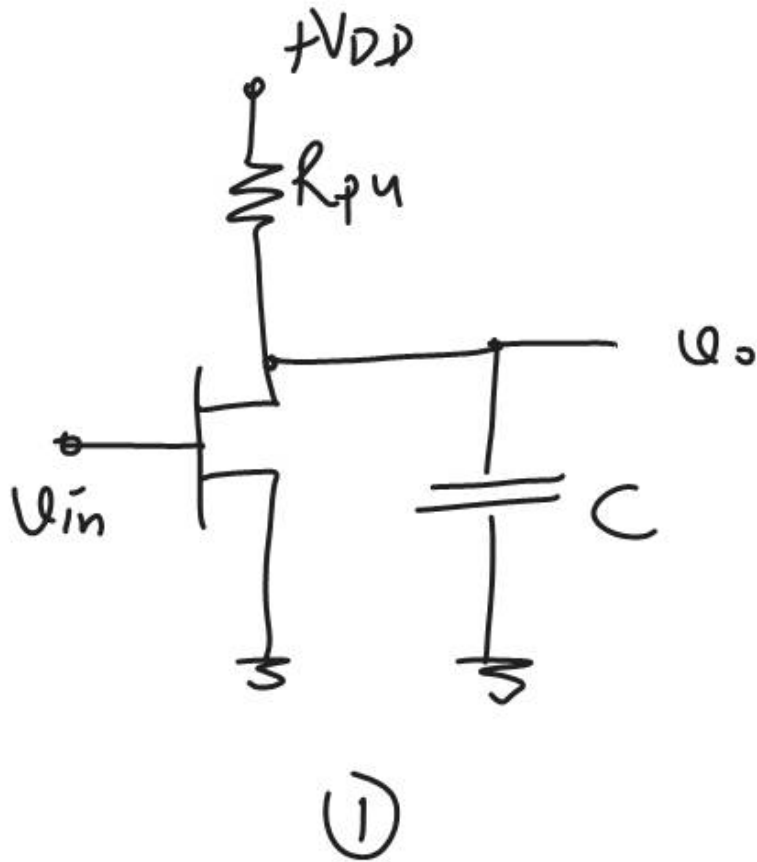

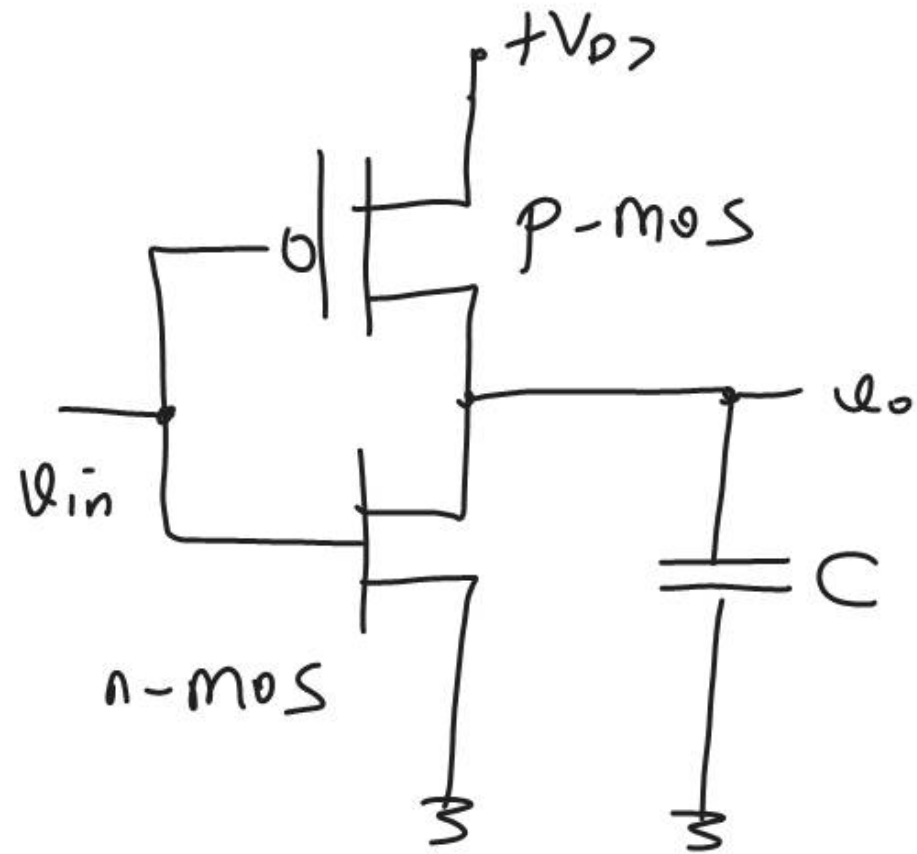


③ CMOS inverter

an-n MOS transistor :

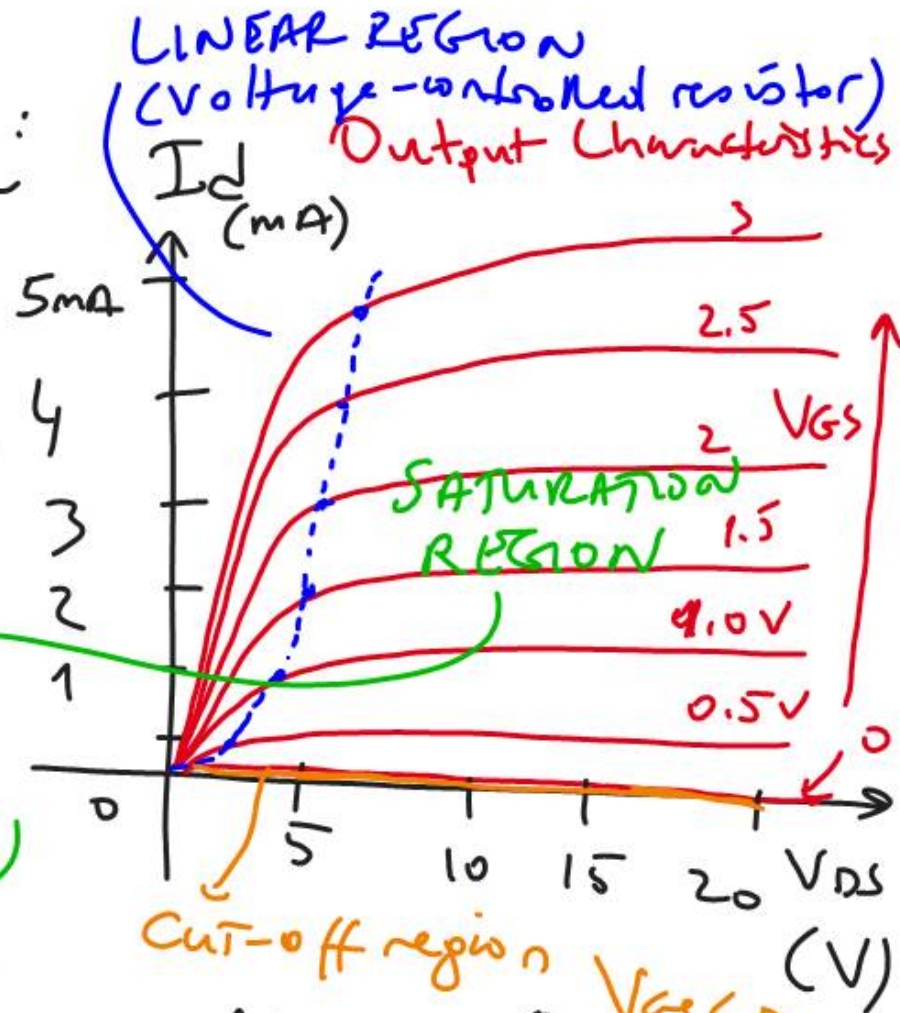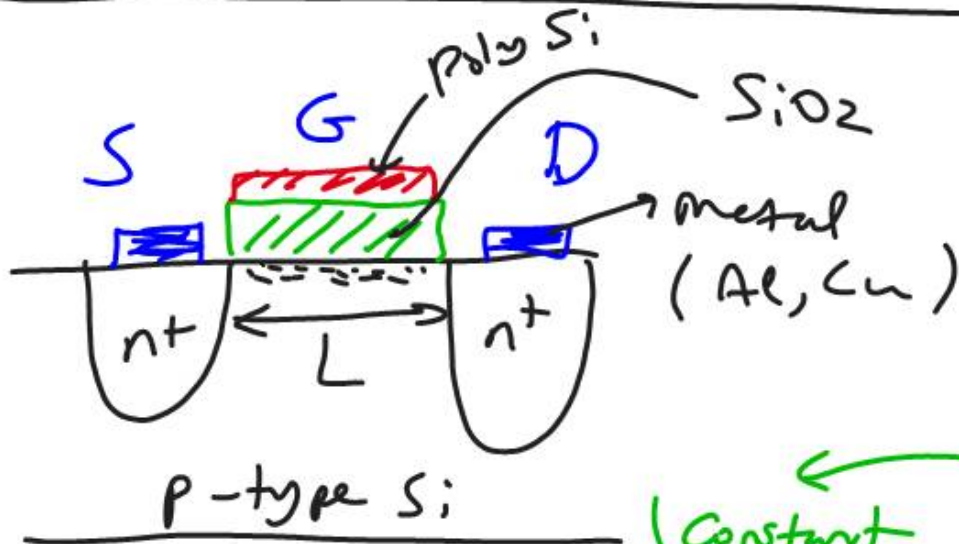

$$\beta = \left(\frac{W}{L} \right) \frac{\mu \cdot \epsilon}{t_{ox}}$$

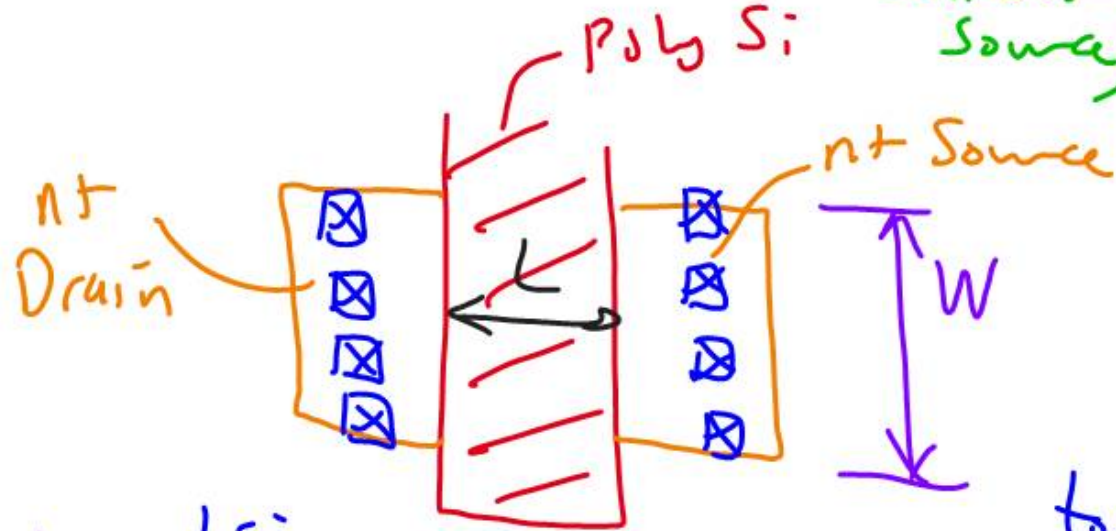t_{ox} is the thickness of Gate oxide (SiO₂) $\approx 50 - 150 \text{ \AA}$



μ : mobility ($\frac{cm^2}{V \cdot s}$)
 ϵ : permittivity F/cm

① Cut-off region

$$I_{ds} = 0 \quad \text{when } V_{gs} \leq V_T \quad \left(V_T = 0 \text{ in the figure above} \right)$$

② Linear Region

$$I_{ds} = \beta \left(V_{gs} - V_T - \frac{V_{ds}}{2} \right) V_{ds} \quad \text{when } V_{gs} - V_T \geq V_{ds}$$

③ Saturation Region

$$I_{ds} = \frac{\beta}{2} (V_{gs} - V_T)^2 \quad \text{when } V_{gs} - V_T < V_{ds}$$

I_{ds} is not a function of V_{ds} .

